

2004年硕士研究生《电路》试题答案

一、解： $\dot{U}_S = 200\sqrt{2}\angle 0^\circ \text{ V}$, $j\omega L = j10^3 \times 1 = j1\text{K}$, $\frac{1}{j\omega C} = -j\frac{1}{10^3 \times 10^{-6}} = -j1\text{K}$

$$(1) \dot{I} = \frac{\dot{U}_S}{-j\frac{1}{\omega C} + (R+j\omega L) \parallel (R+\frac{1}{j\omega C})} = \frac{200\sqrt{2}\angle 0^\circ}{-j1\text{K} + (1\text{K}+j1\text{K}) \parallel (1\text{K}-j1\text{K})} = \frac{200\sqrt{2}\angle 0^\circ}{1\text{K}-j1\text{K}}$$

$$= 0.2\angle 45^\circ \text{ A}$$

$$i(t) = 0.2\sqrt{2} \cos(10^3 t + 45^\circ) \text{ A}$$

$$I = 0.2 \text{ A}$$

$$(2) \dot{U}_{cd} = (R+j\omega L) \parallel (R+\frac{1}{j\omega C}) \dot{I} = 1\text{K} \times 0.2\angle 45^\circ = 200\angle 45^\circ \text{ V}$$


$$\dot{U}_{ab} = \frac{j\omega L}{R+j\omega L} \dot{U}_{cd} - \frac{\frac{1}{j\omega C}}{R+\frac{1}{j\omega C}} \dot{U}_{cd} = \left(\frac{j1\text{K}}{1\text{K}+j1\text{K}} - \frac{-j1\text{K}}{1\text{K}-j1\text{K}} \right) \dot{U}_{cd} = j\dot{U}_{cd}$$

$$= 200\angle 135^\circ \text{ V}$$

$$(3) P = \text{Re}[\dot{U}_S \dot{I}^*] = \text{Re}[200\sqrt{2}\angle 0^\circ \times 0.2\angle -45^\circ] = \text{Re}[40\sqrt{2}\angle -45^\circ]$$

$$= 40 \text{ W}$$

二、解：利用戴维南定理，将左边电路等效

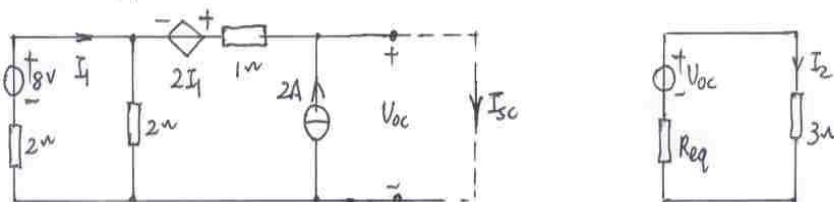

$$V_{oc} = (2+2) \times \frac{8}{2+2} + 2 + 2 \times (-1) + 2 = 10 \text{ V}$$

$$I_{sc} = 10 \text{ A}$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{10 \text{ V}}{10 \text{ A}} = 1 \Omega \text{ (也可利用加压法直接计算)}$$

$$I_2 = \frac{V_{oc}}{R_{eq} + 3} = \frac{10}{1+3} = 2.5 \text{ A}$$

三、解：节点电压方程为 (选结点4为参考结点)

$$\begin{cases} V_{n1} = 4I_1 \\ (\frac{1}{2} + \frac{1}{2} + 1)V_{n2} - \frac{1}{2}V_{n1} - V_{n3} = -2 + 6 \\ V_{n3} = 6 \end{cases}$$

$$\text{又 } I_1 = V_{n2}/2$$

$$\therefore V_{n1} = 20 \text{ V}, V_{n2} = 10 \text{ V}, V_{n3} = 6 \text{ V}$$

$$\text{受控源流出的电流为 } \frac{V_{n1} - V_{n3} + 10}{4} + \frac{V_{n1} - V_{n2}}{2} - 2 = 9 \text{ A}$$

$$\text{受控源的功率为 } P = V_{n1} \times (-1) = -180 \text{ W (发出功率)}$$

四. 解: 根据叠加定理, 互易定理求解.

(1) 根据叠加定理: $V_3 = k_1 V_{s1} + k_2 V_{s2}$

V_{s1} 单独作用, $V_{s2} = 0$ 时, $V_3' = V_1' - V_2' = 8 - 4 = 4V$, $V_3' = k_1 V_{s1}$

$$\therefore 4 = k_1 \times 16 \quad k_1 = \frac{1}{4}$$

(2) 根据互易定理, V_{s1} 接于 V_{s2} 处, V_{s1} 代入的支路接时, 可得

$$V_3'' = V_1'' - V_2'' = 4 - 8 = -4V, \quad V_3'' = k_2 V_{s1}, \quad k_2 = -\frac{1}{4}$$

(3) 由此可得: $V_3 = \frac{1}{4} V_{s1} - \frac{1}{4} V_{s2}$ (V_{s1}, V_{s2} 共同作用时)

且 $V_3 = -8V$ 时, $-8 = \frac{1}{4} \times 16 - \frac{1}{4} \times V_{s2}$

$$\therefore V_{s2} = 48V$$

五. 解: 设并联部分电压为 $\dot{U}_1 = U_1 \angle 0^\circ V$, 则 $\dot{U} = 220 \angle \varphi$,

$$U_1 = \sqrt{R^2 + (\omega L)^2} \times I_1 = \sqrt{10^2 + 10^2} \times 10\sqrt{2} = 200V$$

$$\therefore \dot{U}_1 = 200 \angle 0^\circ V$$

$$\dot{I}_1 = 10\sqrt{2} \angle 45^\circ A, \quad \dot{I}_2 = 10 \angle 90^\circ A$$


$$\dot{I} = \dot{I}_1 + \dot{I}_2 = 10\sqrt{2} \angle 45^\circ + 10 \angle 90^\circ = 10 \angle 0^\circ A$$

$$\text{由 } R_1 \dot{I} + \dot{U}_1 = \dot{U} \Rightarrow 10R_1 \angle 0^\circ + 200 \angle 0^\circ = 220 \angle \varphi \Rightarrow \varphi = 0^\circ$$

$$R_1 = (220 - 200) / 10 = 2 \Omega$$

$$P = \text{Re}[\dot{U} \dot{I}^*] = \text{Re}[220 \angle 0^\circ \times 10 \angle 0^\circ] = 2200 W$$

六. 解: 原电路去耦等效的相量模型如下图所示

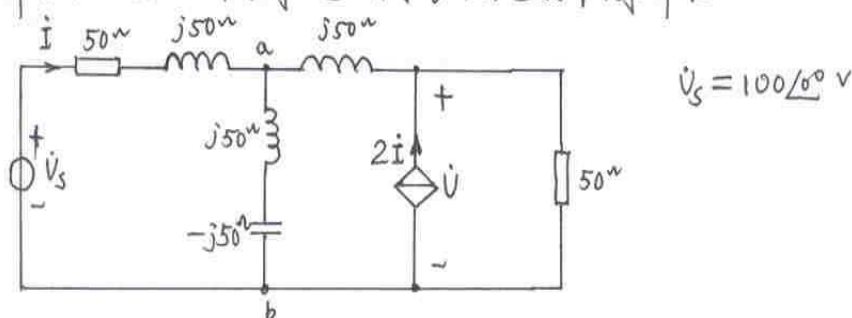


图中, a, b 两点等效阻抗为容, 两点等电位, $U_{ab} = 0$.

$$\dot{I} = \frac{100 \angle 0^\circ}{50 + j50} = \sqrt{2} \angle 45^\circ A$$

$$\dot{U} = (50 // j50) \times 2\dot{I} = \frac{50j}{1+j} \times 2 \times \sqrt{2} \angle 45^\circ = 100 \angle 0^\circ V$$

七, 解: 先将右边部分等效得到下图.

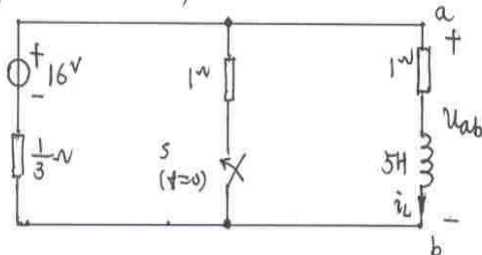

$$i_L(0_-) = \frac{16}{\frac{1}{3} + 1} = 12 \text{ A}$$

再利用三要素法求解.

$$\textcircled{1} U_{ab}(0_+) = \frac{16 \times 3 - 12}{3 + 1} = 9 \text{ V}$$

$$\textcircled{2} U_{ab}(\infty) = \frac{16 \times 3}{3 + 1 + 1} = 9.6 \text{ V}$$

$$\textcircled{3} \tau = L/R_{eq} = 5 / (5/4) = 4 \text{ s, 其中 } R_{eq} = 1 + 1 // (\frac{1}{3}) = \frac{5}{4} \Omega$$

$$U_{ab}(t) = 9.6 + (9 - 9.6)e^{-\frac{t}{4}} = 9.6 - 0.6e^{-\frac{t}{4}} \text{ V } t \geq 0$$

八, 解: 首先求出 a, b 右侧电路的戴维南等效电路

$$V_{oc(ab)} = \frac{-I_s + \frac{2I_s}{R_1 + j\omega L}}{\frac{1}{R_1 + j\omega L} + \frac{1}{R_2 + \frac{1}{j\omega C}}} = \frac{-I_s + \frac{2}{1+j}I_s}{\frac{1}{1+j} + \frac{1}{1-j}} = -I_s + (1-j)I_s = -jI_s$$

$$I_{sc(ab)} = \frac{2I_s}{R_1 + j\omega L} - I_s = \frac{2}{1+j}I_s - I_s = -jI_s$$

$$Z_{eq} = \frac{V_{oc(ab)}}{I_{sc(ab)}} = 1 \Omega$$

(1) 当 $Z_L = Z_{eq}^* = 1 \Omega$ 时, 即 $Z_L = \frac{1}{4} Z_L' = \frac{1}{4} \Omega$ 时, Z_L 可从电路获得最大功率.

$$(2) \text{ 最大功率 } P_{max} = \frac{V_{oc}^2}{4\text{Re}[Z_{eq}]} = \frac{I_s^2}{4 \times 1} = \frac{20^2}{4} = 100 \text{ W}$$

九, 解: (1) 由仪表的读数

$$I = \frac{380/\sqrt{2}}{|Z|} = \frac{220}{|16 + j12|} = 11 \text{ A}$$

(2) 三相负载吸收的总功率

$$P = 3 \times I^2 \times \text{Re}[Z] = 3 \times 11^2 \times 16 = 5808 \text{ W}$$

(3) 并联 Δ 型电容网络的功率因数

$$Q = 3 \times I^2 \times \text{Im}[Z] - 3 \times \omega C \times 380^2 = 3 \times 11^2 \times 12 - 3 \times 314 \times 30 \times 10^{-6} \times 380^2$$

$$= 4356 - 4080.744 \approx 275 \text{ Var}$$

$$\varphi = \text{tg}^{-1} \frac{Q}{P} = \text{tg}^{-1} \frac{275}{5808} = \text{tg}^{-1} 0.0474 = 2^\circ 43'$$

$$\cos \varphi \approx 1$$

$$\text{+. 解: } \begin{cases} u_1 \\ i_1 \end{cases} = \begin{bmatrix} 2.5 & 3 \\ 0.5 & 2 \end{bmatrix} \begin{cases} u_2 \\ -i_2 \end{cases} \quad \therefore \begin{cases} u_1 = 2.5u_2 - 3i_2 \\ i_1 = 0.5u_2 - 2i_2 \end{cases}$$

① $u_3(t)$ 中 10V 直流作用时, L_1, L_2 短路, $u_2^{(0)} = 0$

$$\begin{cases} u_1^{(0)} = -3i_2^{(0)} \\ i_1^{(0)} = -2i_2^{(0)} \end{cases} \quad \text{又 } u_1^{(0)} = 10 - i_1^{(0)}$$

$$\therefore i_2^{(0)} = -2\text{A}$$

② $u_3(t)$ 中 $100\sqrt{2} \cos \omega t$ 作用时, C 与 L_2 的并联等效导纳

$$Y = j\frac{1}{6} + \frac{1}{j6} = 0 \quad \text{即 } C \text{ 与 } L_2 \text{ 发生并联谐振}$$

$$i_2^{(1)} = 0$$

③ $u_3(t)$ 中 $10\sqrt{2} \cos 3\omega t$ 作用时, $\dot{U}_S^{(3)} = 10\angle 0^\circ \text{V}$

$$\therefore 2.2' \text{ 右侧等效阻抗为 } Z = j3 \times 0.75 + (j3 \times 6) / (-j6/2) = 0$$

$$\therefore 2.2' \text{ 右侧发生串联谐振 } \dot{U}_2^{(3)} = 0$$

$$\text{故有 } \begin{cases} \dot{U}_1^{(3)} = -3\dot{I}_2^{(3)} \\ \dot{I}_1^{(3)} = -2\dot{I}_2^{(3)} \end{cases} \quad \text{又 } \dot{U}_1^{(3)} = \dot{U}_S^{(3)} - \dot{I}_1^{(3)}$$

$$\therefore \dot{I}_2^{(3)} = 2\angle 180^\circ \text{A} = -2\text{A}$$

$$i_2(t) = -2 + 2\sqrt{2} \cos(3\omega t + 180^\circ) \text{A}$$

$$I_2 = \sqrt{(-2)^2 + 2^2} = 2\sqrt{2} \text{A}$$