

2006年硕士研究生《电路》试题参考答案

一、解：结点电压方程为

$$\begin{cases} \frac{1}{5}u_{n1} - \frac{1}{5}u_{n2} = 5 - I \\ u_{n2} = 5I \\ -\frac{1}{6}u_{n2} + (\frac{1}{6} + \frac{1}{8})u_{n3} = I \end{cases} \quad \text{补充: } \begin{cases} u_{n1} - u_{n3} = 4 \\ I = \frac{1}{8}u_{n3} \end{cases}$$

解得:  $u_{n1} = 20V, u_{n2} = 10V, u_{n3} = 16V, I = 3A$   
 $P = 4I = 12W$  (吸收)


二、解：根据叠加定理，求

$$I = k_1 I_s + k_2 U_s = 2I_s - 0.1U_s$$

其中:  $\begin{cases} 1 = k_1 + 10k_2 \\ 4.5 = 2k_1 - 5k_2 \end{cases} \Rightarrow k_1 = 2, k_2 = -0.1$

当  $U_s = 15V, I_s = 2.5A$  时,  $I = 2 \times 2.5 - 0.1 \times 15 = 3.5A$

三、解: S1: 求  $R_L$  左边电路的戴维南等效电路

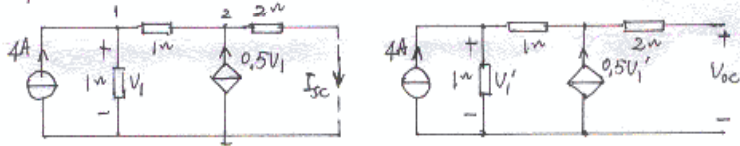

①  $I_{sc} = \frac{1}{2}V_2 = 2A, \begin{cases} 2V_1 - V_2 = 4 \\ -V_1 + 1.5V_2 = 0.5V_1 \end{cases}$  (结点方程)  $\Rightarrow V_1 = V_2 = 4V$

②  $V_{oc} = 0.5V_1 + 1.0V_1 = 12V, \therefore V_1 = 4 + 0.5V_1 \Rightarrow V_1 = 8$

③  $R_{eq} = V_{oc}/I_{sc} = 6\Omega$

S2:  $R_L = R_{eq} = 6\Omega$  时,  $R_L$  获得最大功率


$$P_{max} = \frac{V_{oc}^2}{4R_{eq}} = \frac{12^2}{4 \times 6} = 6W$$

四、解: S1: 因已知  $\dot{U}$  与  $\dot{I}$  同相, 而  $\dot{U} = RI + \dot{U}_c$ , 因此可知,  $\dot{U}_c$  与  $\dot{I}$  同相, 可作出如右图所示相量图。

相量图

$\dot{U} = 220\angle 0^\circ V, \dot{U}_c = U_c\angle 0^\circ, \dot{I} = I\angle 0^\circ A$

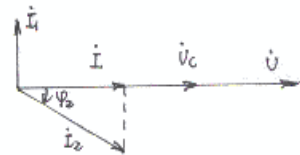$\dot{I}_1 = 10\angle 90^\circ A, \dot{I}_2 = 20\angle 45^\circ A$



∴  $I_1 + I_2 \sin \varphi_2 = 0, \Rightarrow \varphi_2 = -30^\circ, I = I_2 \cos 30^\circ = 10\sqrt{3} \text{ A}$

s2: 因  $Z_2$  上消耗功率为  $P_2 = 2 \text{ kW}$ , 故有

$$V_C = \frac{P_2}{I_2 \cos \varphi_2} = \frac{2 \times 10^3}{20 \times \cos 30^\circ} = 115.5 \text{ V}$$

$$X_C = \frac{V_C}{I_1} = \frac{115.5}{10} = 11.55 \Omega$$

$$Z_2 = \frac{V_C}{I_2} = \frac{115.5 \angle 0^\circ}{20 \angle -30^\circ} = 5.77 \angle 30^\circ \Omega = 5 + j2.89 \Omega$$


$$R = \frac{V_R}{I} = \frac{104.5 \angle 0^\circ}{10\sqrt{3}} = 6.04 \Omega \text{ (其中 } V_R = V - V_C = 104.5 \angle 0^\circ \text{ V)}$$

五. 解: s1: 设  $\dot{U}_S = 100 \angle 0^\circ \text{ V}$ , 根据已知条件, 可得如下相量图.

相量图:

$$\dot{I}_C = \frac{\dot{U}_S}{-jX_C} = 10 \angle 90^\circ \text{ A}, \dot{I}_L = \frac{\dot{U}_S}{R_L + jX_L} = I_L \angle \varphi_L \text{ A}$$
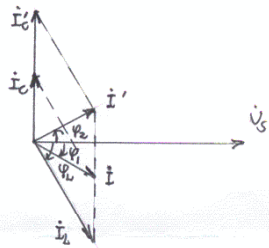
$$\dot{I} = 10 \angle \varphi_1 \text{ A}, \dot{I}' = 20 \angle 90^\circ \text{ A}, \dot{I}' = 1 \angle \varphi_2 \text{ A}$$



满足上列条件时, 可求出

$$\varphi_L = -60^\circ, \varphi_1 = -30^\circ, \varphi_2 = 30^\circ$$

$$\therefore I \cos 30^\circ = I_L \cos 60^\circ$$


$$\therefore I_L = \sqrt{3} I = 10\sqrt{3} \text{ A}$$

$$\text{s2: } I_L = \frac{U_S}{\sqrt{R_L^2 + X_L^2}} \Rightarrow \sqrt{R_L^2 + X_L^2} = \frac{10}{\sqrt{3}}, \text{ 又 } \frac{X_L}{R_L} = \tan(-\varphi_L) = \sqrt{3}$$


$$\therefore \sqrt{R_L^2 + X_L^2} = 2R_L \Rightarrow R_L = \frac{5}{\sqrt{3}} \Omega, X_L = 5 \Omega$$

$$\text{s3: } P = I_L^2 \times R_L = (10\sqrt{3})^2 \times \frac{5}{\sqrt{3}} = 500\sqrt{3} = 866 \text{ W}$$

六. 解: 先作出去耦等效电路, 再分别计算基波作用和二次谐波作用的电路.

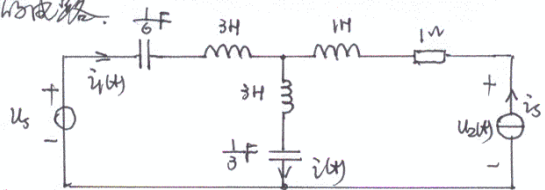

s1: 基波作用, 相量模型如下图. 则有

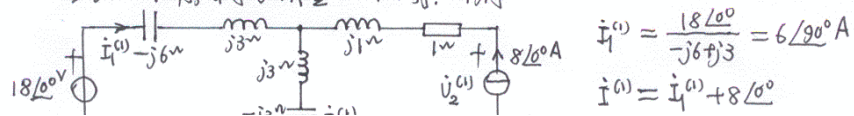


$$\dot{I}_1^{(1)} = \frac{18 \angle 0^\circ}{-j6 + j3} = 6 \angle 90^\circ \text{ A}$$

$$\dot{I}_2^{(1)} = \dot{I}_1^{(1)} + 8 \angle 0^\circ$$

$$\dot{U}_2^{(1)} = 8\angle 0^\circ \times (1+j1) = 8\sqrt{2} \angle 45^\circ \text{ V}$$

$$\dot{i}^{(1)} = 10\sqrt{2} \cos(\omega t + 36.9^\circ) \text{ A}$$

s2: 二次谐波作用, 相量模型如下图. 则有

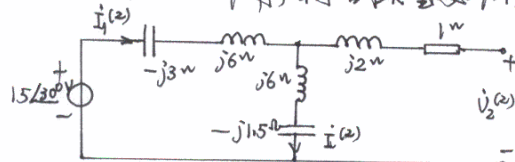

$$\dot{i}^{(2)} = \frac{15\angle 30^\circ}{-j3 + j6 + j6 - j1.5}$$

$$= 2\angle 60^\circ \text{ A}$$

$$\dot{i}^{(2)} = \dot{i}_1^{(2)} = 2\angle 60^\circ \text{ A}$$

$$\dot{U}_2^{(2)} = 2\angle 60^\circ (j6 - j1.5) = 9\angle 30^\circ \text{ V}$$

$$i^{(2)} = 2\sqrt{2} \cos(2\omega t - 60^\circ) \text{ A}$$


s3) 总电流  $i(t) = i^{(1)} + i^{(2)} = 10\sqrt{2} \cos(\omega t + 36.9^\circ) + 2\sqrt{2} \cos(2\omega t - 60^\circ) \text{ A}$

s4) 电源发出的功率分别为

$$P_{13} = 18 \times 6 \times \cos 90^\circ + 2 \times 9 \times \cos 90^\circ = 0$$

$$P_{15} = 8\sqrt{2} \times 8 \times \cos 45^\circ = 64 \text{ W}$$

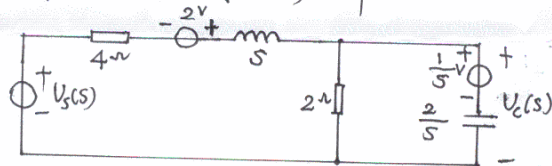七, 解: 运算电路如下图所示, 其中  $U_5(s) = \mathcal{L}[2\varepsilon(t)] = \frac{2}{s} \text{ V}$



列节点电压方程为

$$\left(\frac{1}{s+4} + \frac{1}{2} + \frac{s}{2}\right) U_6(s) = \frac{U_5(s) + 2}{s+4} + \frac{1}{s}$$


$$\therefore U_6(s) = \frac{\frac{4}{s} + s + 8}{(s+2)(s+3)} = \frac{s^2 + 8s + 4}{s(s+2)(s+3)}$$

$$= \frac{2}{3} \times \frac{1}{s} + 4 \times \frac{1}{s+2} - \frac{11}{3} \times \frac{1}{s+3}$$

$$\therefore u_6(t) = \left(\frac{2}{3} + 4e^{-2t} - \frac{11}{3}e^{-3t}\right) \varepsilon(t) \text{ V}$$

八, 解: s1:  $i_1(0_-) = \frac{12}{4/4} = 6 \text{ A}$ ,  $u_6(0_-) = r i_1(0_-) + R_2 \times \frac{i_1(0_-)}{2} = 4 i_1(0_-) = 24 \text{ V}$

s2: 运算电路如下图所示,

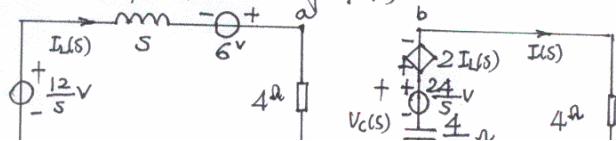

$$S3: \therefore (4+s)I_L(s) - 6 - \frac{12}{s} = 0$$

$$\therefore I_L(s) = \frac{1}{4+s} \left( \frac{12}{s} + 6 \right) = \frac{6s+12}{s(s+4)} = \frac{3}{s} + \frac{3}{s+4}$$

$$i_L(t) = \mathcal{L}^{-1}[I_L(s)] = (3 + 3e^{-4t}) \varepsilon(t) \text{ A}$$

$$S4: \therefore \left(4 + \frac{4}{s}\right)I(s) - \frac{24}{s} + 2I(s) = 0, \quad \text{且 } U_0(s) = \frac{24}{s} - \frac{4}{s}I(s)$$

$$\begin{aligned} \therefore U_0(s) &= \frac{24}{s} - \frac{4}{s} \times \frac{s}{4(s+1)} \left( \frac{24}{s} - 2I(s) \right) = \frac{24}{s} - \frac{24}{s(s+1)} + \frac{2}{s}I(s) \\ &= \frac{24}{s+1} + \frac{2(6s+12)}{s(s+1)(s+4)} = \frac{20}{s+1} + \frac{6}{s} - \frac{2}{s+4} \end{aligned}$$

$$u_0(t) = \mathcal{L}^{-1}[U_0(s)] = (6 + 20e^{-t} - 2e^{-4t}) \varepsilon(t) \text{ V}$$

$$S5: \therefore U_{ab}(s) = 4I_L(s) - U_0(s) + 2I_L(s) = 6I_L(s) - U_0(s)$$

$$\begin{aligned} \therefore u_{ab}(t) &= \mathcal{L}^{-1}[U_{ab}(s)] = 6i_L(t) - u_0(t) = (18 + 12e^{-t} - 6 - 20e^{-t} + 2e^{-4t}) \varepsilon(t) \\ &= (12 - 20e^{-t} + 2e^{-4t}) \varepsilon(t) \text{ V} \end{aligned}$$

九、解：由传输参数矩阵可得

$$\begin{cases} U_1 = 2U_2 - 6I_2 \\ I_1 = 0.5U_2 - 1.5I_2 \end{cases} \Rightarrow \begin{cases} I_2 = 0 \text{ 时, } U_{oc} = U_2 = \frac{1}{2}U_1 = 6 \text{ V} \\ U_2 = 0 \text{ 时, } I_{sc} = -I_2 = \frac{1}{6}U_1 = 2 \text{ A} \end{cases}$$

$$\therefore R_{eq} = U_{oc}/I_{sc} = 3 \Omega$$

故：1) 当  $R = R_{eq} = 3 \Omega$  时，获得最大功率， $P_{max} = \frac{U_{oc}^2}{4R_{eq}} = \frac{6^2}{4 \times 3} = 3 \text{ W}$

2)  $U_2$  的功率  $P_{U_2} = -U_2 I_2 = -12 [0.5 \times 3 - 1.5 \times (-1)] = -36 \text{ W}$  (发出)

十、解：S1: 设负载端相电压  $\dot{U}_{AN'} = 220 \angle 0^\circ \text{ V}$ ，则有

$$I_A = \frac{P}{\sqrt{3} U_{AB} \cos \varphi} = \frac{760\sqrt{3}}{\sqrt{3} \times 380 \times 0.707} = 2\sqrt{2} \text{ A}, \quad \text{另 } \varphi = 45^\circ$$

$$\therefore \dot{I}_A = 2\sqrt{2} \angle 45^\circ \text{ A}$$

$$S2: \text{电源端相电压 } \dot{U}_A = Z_1 \dot{I}_A + \dot{U}_{AN'} = \sqrt{2} \angle 45^\circ \cdot 2\sqrt{2} \angle 45^\circ + 220 \angle 0^\circ = 224 \angle 0^\circ \text{ V}$$

$$\text{电源端线电压 } \dot{U}_{AB} = \sqrt{3} \dot{U}_A \angle 30^\circ = 388 \angle 30^\circ \text{ V}$$

$$\begin{aligned} S3: \text{功率表的读数 } P &= \operatorname{Re}[\dot{U}_{BC} \dot{I}_A^*] = \operatorname{Re}[\dot{U}_{AB} \angle 120^\circ \dot{I}_A^*] \\ &= \operatorname{Re}[\sqrt{3} \dot{U}_A \angle 90^\circ \dot{I}_A^*] = \operatorname{Re}[\sqrt{3} \dot{U}_A \dot{I}_A^* \angle 90^\circ] \\ &= \sqrt{3} U_A I_A \cos(45^\circ - 90^\circ) = 776 \text{ W} \end{aligned}$$

S4: 无功功率表的读数可表示为  $P = \operatorname{Re}[\sqrt{3} \dot{U}_A \dot{I}_A^* \angle 90^\circ]$

$$\begin{aligned} \therefore P &= \sqrt{3} U_A I_A \cos(\varphi - 90^\circ) = \sqrt{3} U_A I_A \sin \varphi \\ &= U_{AB} I_A \sin \varphi \end{aligned}$$